

Outline of Lecture

- **Main Memory**
- **Building a Datapath**

Main Memory


- A register file is a fast small amount of memory inside the processor.
- Larger amount of memory which resides outside the processor are built either using SRAMs (Static Random Access Memory) or DRAMs (Dynamic Random Access Memory).
- SRAMs (They are typically built using flip-flops) do not need to be *refreshed* periodically like DRAMs (They are typically built using capacitors) - but are more expensive and less dense.
- SRAMs are used for small memories (e.g., Cache), and DRAMs are used for large memories (e.g., main memory).

Example

a 256K x 1 SRAM contains 256K entries, and each entry is 1 bit wide.


Thus we need 18 address lines (i.e., $2^{18} = 256K$).

 - A 32K x 8 SRAM has the same number of bits, but will have 15 address lines (to address 32K entries) and each entry holds 8 bits.




Decoder

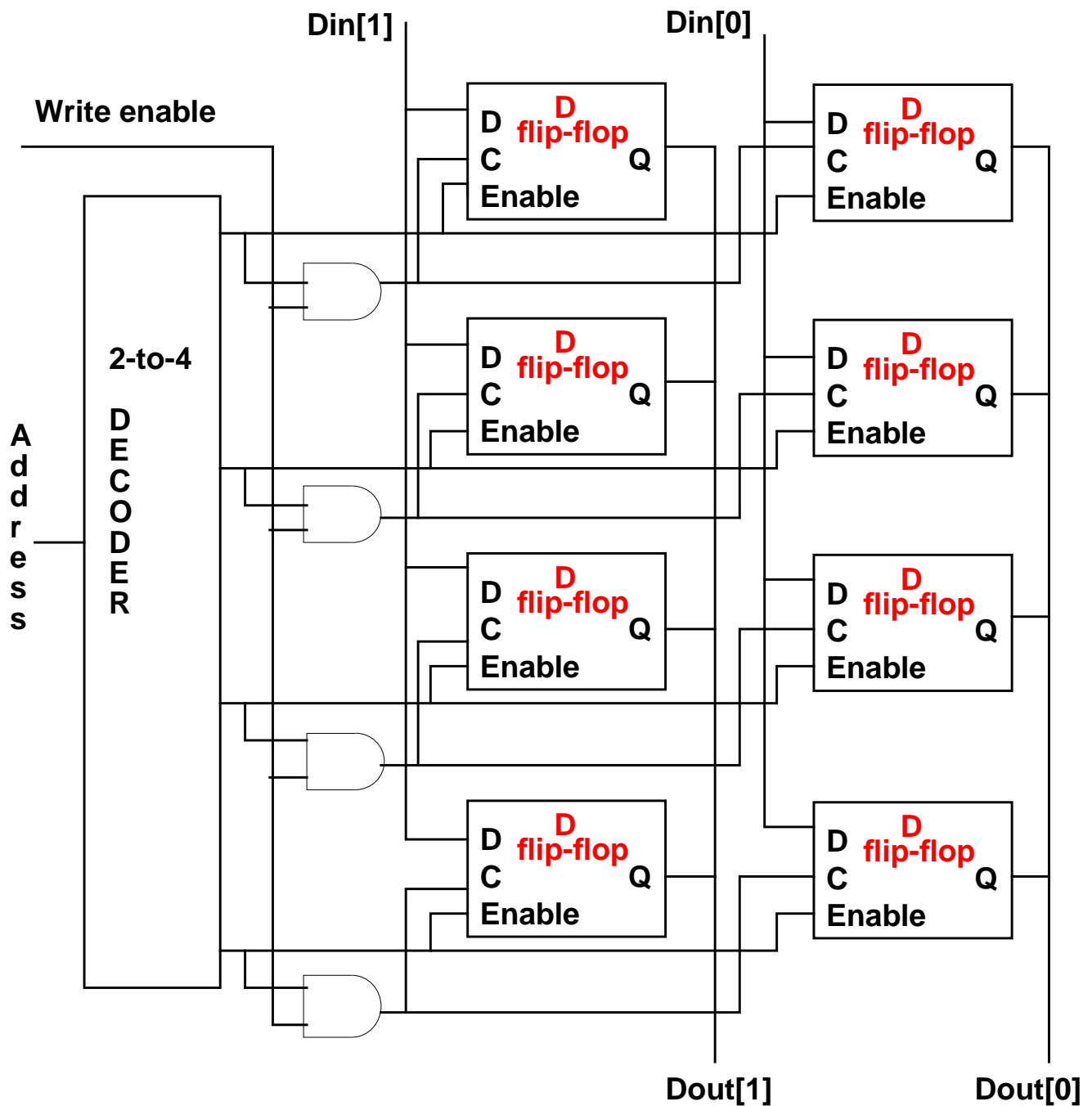- In order to activate individual words within a SRAM, we need a *decoder* to accomplish that.




Two-Step Decoder

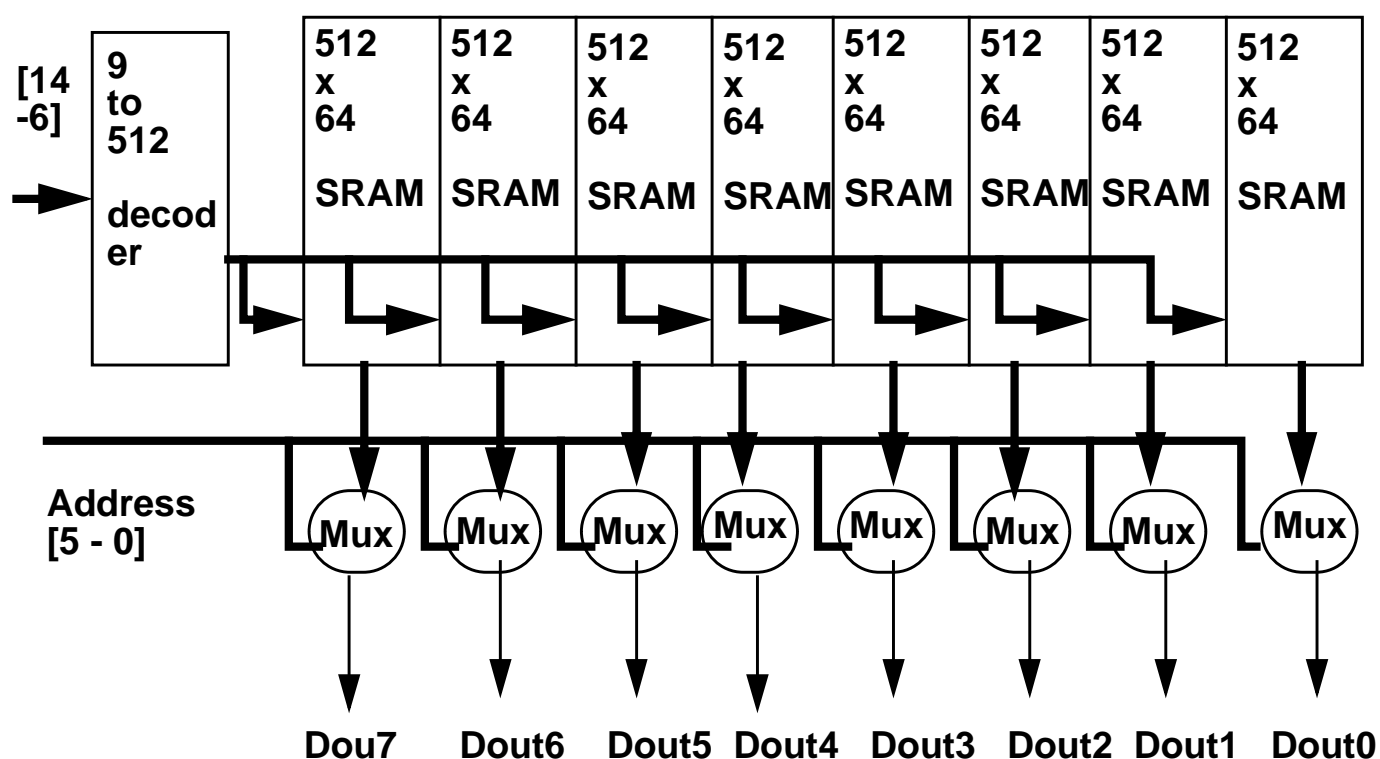- In order to solve the problem of having large decoders for large memories, a two-step decoding process can be used:




Building a Datapath

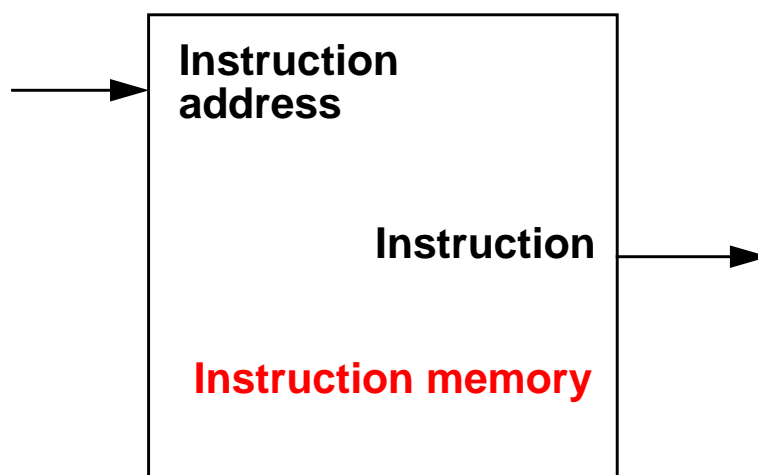
- In designing our datapath, we initially assume that each MIPS instruction takes a single clock cycle. Later, we will look at the more realistic case, where each instruction takes a variable number of clock cycles.
- The first element we need in a data path is a memory unit to store the instructions in a program and supply an instruction given its address.



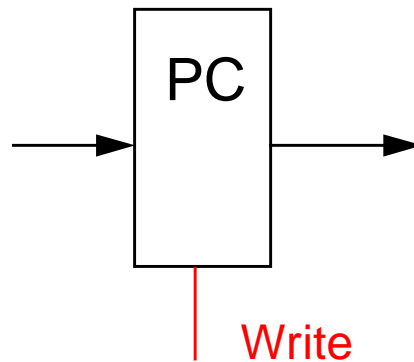
- The address of the instruction being executed is also stored in a register called program counter (**PC**).



 - We need to be able to increment the PC to point to the next instruction. This can be done using the ALU we designed in the previous chapter.



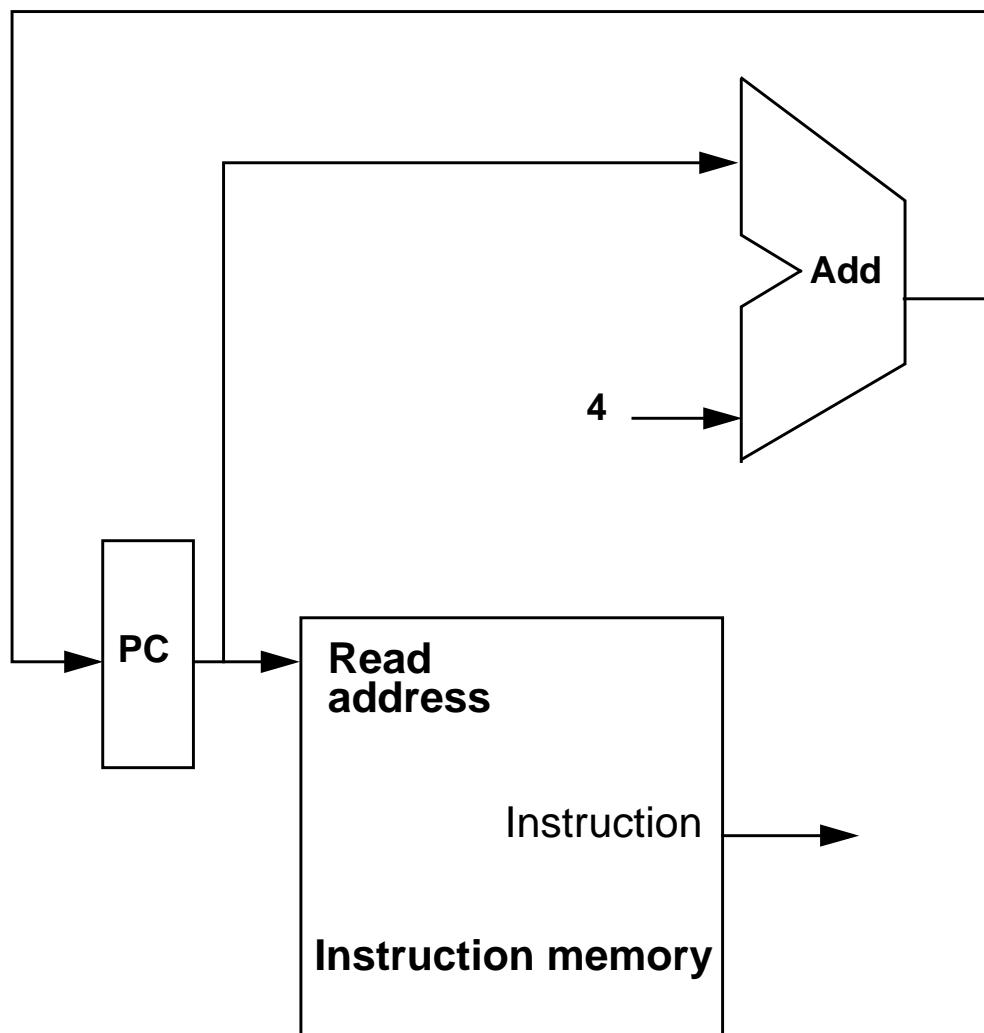- In order to execute an instruction, we need to **fetch** the instruction, and **increment** (+ 4) the program counter so that it is ready for the next instruction.




- Next we consider the execution of *R-format instructions* (R-type instructions). They all read two registers, perform an ALU operation (add, sub, and, or, and slt) and write the result into a register.


op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

- **To read:** We need an input to the register file that specifies the register number (5 bits) to be read and an output (32 bits) that will carry the value read.
- **To write:** We need to specify the register number to be written, and we need to input the data (32 bits) that will be written into that register.

∴ We need a total of 4 inputs

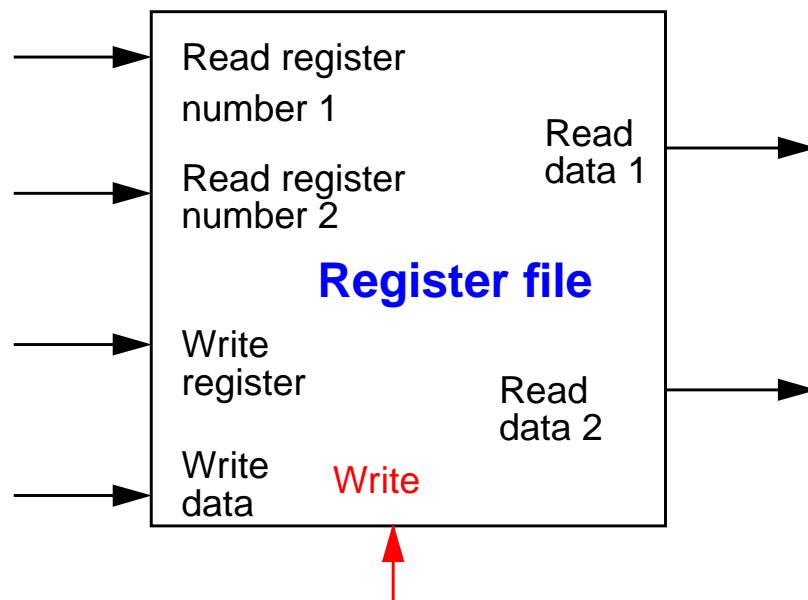


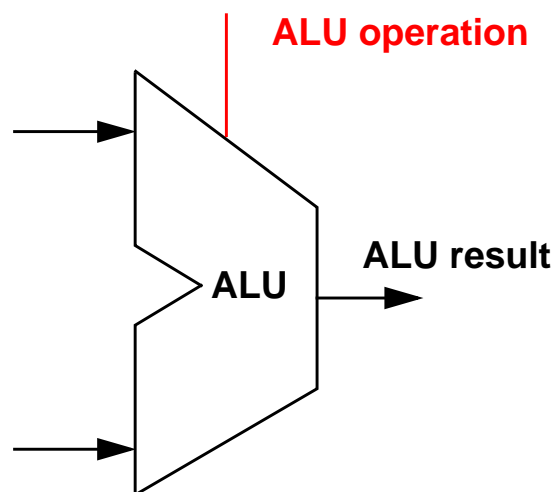- The ALU takes two 32-bit inputs and produces a 32-bit result - it is controlled by a **3-bit signal** as described in our previous lectures.



The Data Path for R-type Instructions

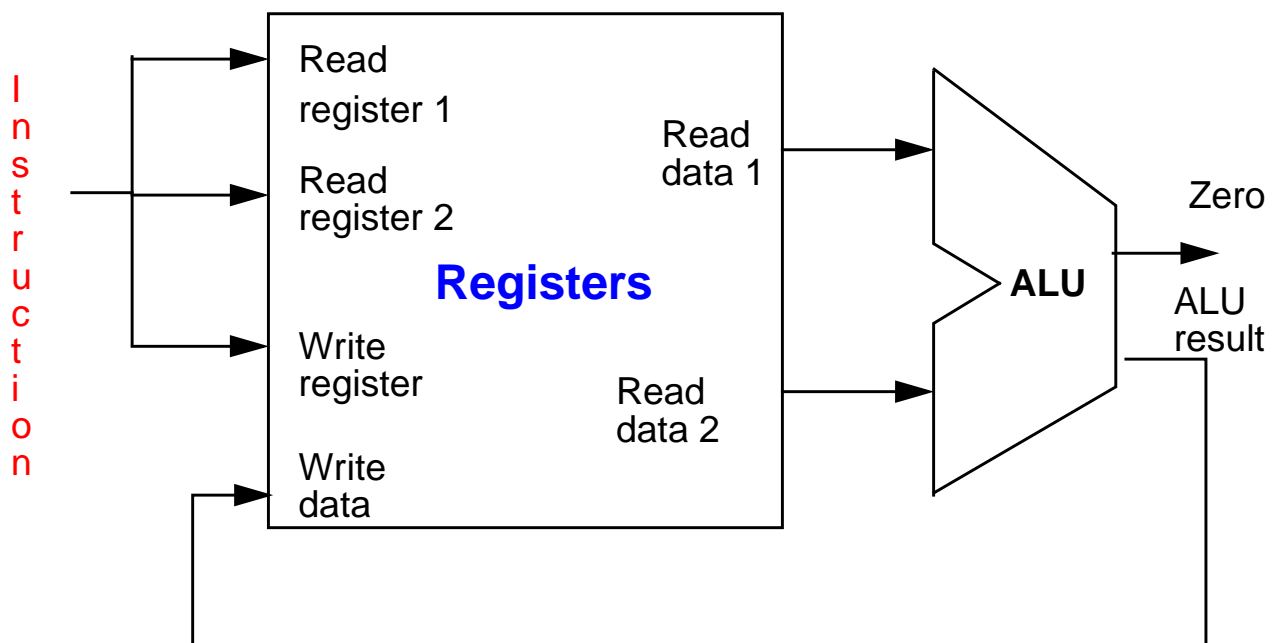- The Data path for R-type instructions is as follows:



Further Reading

Chapter 5 & Appendix B. David A. Patterson and John L. Hennessy. *Computer Organization & Design: The Hardware / Software Interface*. Morgan Kaufman Publishers, 1998. (343-348 and B-28 to B-33).